

The Mains Attraction





**Be safe and test your mains sockets with this very simple gadget.
A mini project by Mark Price**

You know the situation - you've spent all day knocking channels and holes in the plaster, and burying the cables. It's now nearly midnight, and you're just fitted the socket plates and turned the power back on. You could get the multimeter out and check it's all wired correctly, but you really can't be bothered. After all you joined the three wires to the right terminals didn't you? And the earth wire didn't come away when you screwed the plate in place, did it? Can you be certain it's correct?

Wouldn't it be useful to have a little whistles that you can plug into the socket, and that'll tell you instantly if it's wired OK or not. A professional electrician would have a test plug with three neon lights to do just this. However these items are not readily

available in
DIY stores.

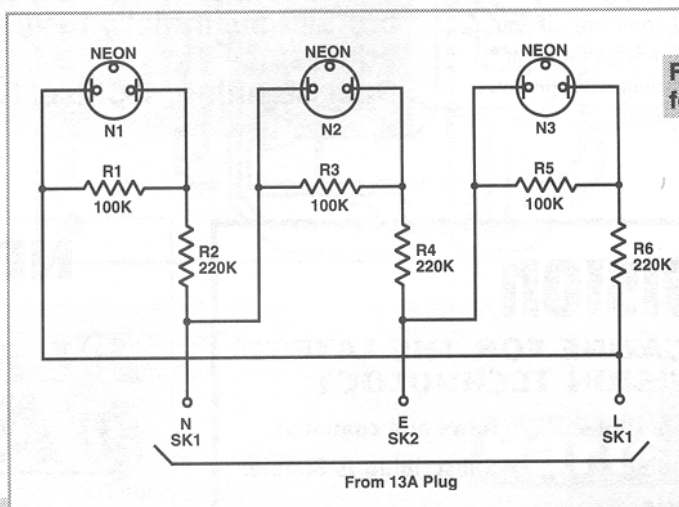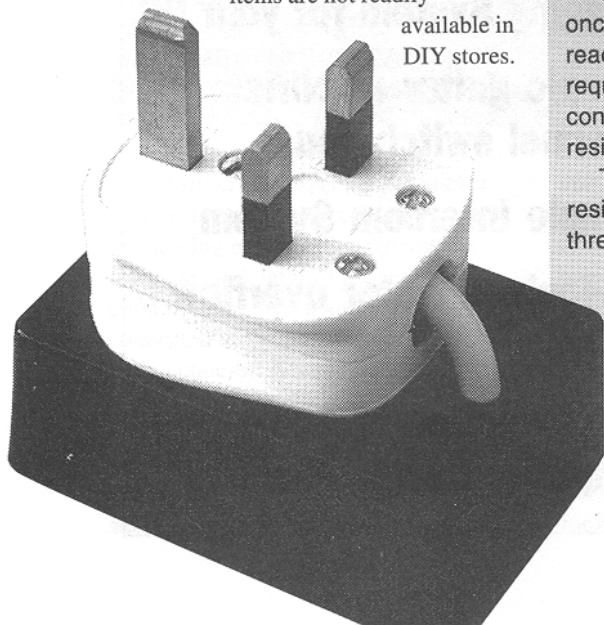

**Fig.1 Circuit
for tester**

The Works

The complete circuit diagram is shown in Figure 1.

The neon lamps will illuminate once the voltage across them reaches about 70V. The current required is less than 1mA, which is controlled by the series 220K resistor.

Three sets of neon and series resistor is connected between the three pins on a 13A plug. With a correctly wired socket, the Live to Neutral and Live to Earth

neons only, will light.

The additional 100K resistors in parallel with each neon prevent the neons lighting if there are two in series. This would happen if the Earth or Neutral wire was not connected.

This unit can reveal all common socket wiring errors, except Neutral and Earth reversed. Since these two lines are at almost the same potential this is impossible to detect with a simple testplug.

You can get them from electrical trade counters and wholesalers, but they cost around £40, which is rather expensive for the occasional DIY job.

The testplug described here does

exactly the same job as the professional ones - and works the same way. However this one uses about six pounds worth of readily obtainable bits.

The testplug is also useful for checking multiway adaptors and

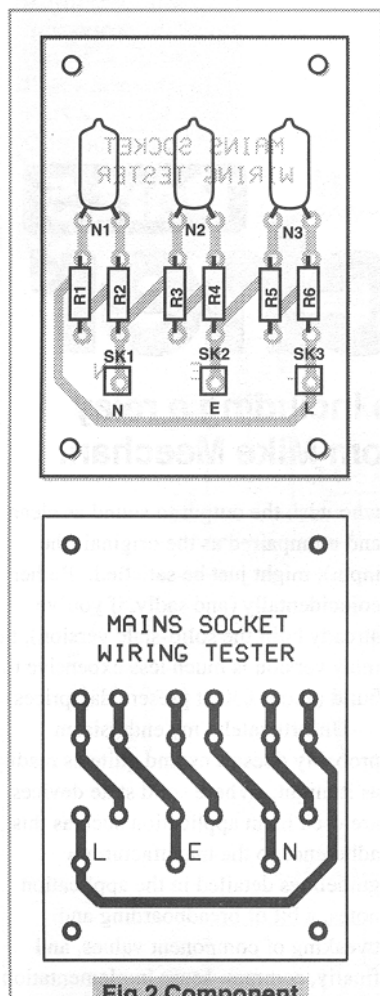


Fig.2 Component positioning and foil pattern

extension leads. Earth faults are surprisingly common with these, and will normally pass unnoticed until the worst happens.

Construction

The neons and resistors are mounted on a small PCB, which is available from the EIA PCB service. The component positioning is shown in Figure 2.

Before fitting the neons, attach a white self adhesive label to the PCB, with the bottom edge 5mm above the neon holes. This is to reflect the light from the neons. Bend the neon leads 5mm from the body before fitting into the PCB. Although the PCB assembly is straightforward, please take care to avoid errors.

The PCB is fitted into a small plastic box (type T3), which is mounted on the back of a normal 13A plug. The original plan was to use one of the small cases fitted with plug pins, intended for small power supplies. However these are not readily available with a metal earth pin.

Select a 13A plug with a flat back (many are slightly curved). Ideally this should be made of the softer unbreakable plastic, since this is easier

to drill. The plug used on the prototype originated from the far east and was branded PMS.

Remove the back from the plug, and drill two 3mm holes in convenient positions. On the prototype, one hole was above the cord grip and the other was in the void between the Neutral and Earth pins.

Position the plug back on the base of the box, about 5mm down from the top, and mark the positions of the holes. Drill the holes and fix the plug back in place with two 6mm long M3 screws and suitable nuts. Drill a hole in the back of the box, below the plug cable entry position, to suit the three core being used.

Take a 100mm length of this flex and connect one end correctly to the plug base. Fit a 3 Amp or lower fuse in the plug. Feed the other end of the wire through the hole in the box, and screw the plug together. Fit a cable tie around the cable on the inside of the box. Strip the outer insulation back, inside the box.

Position the PCB centrally inside the box lid. Mark and drill the four 3mm fixing holes and three 6mm holes for the neons to show through. If a piece of clear or red filter material is available this should be glued inside the case over the holes.

If the unit is correctly assembled there is no reason why it should not work first time

Cut the wires to length and solder to the PCB as shown on the component overlay. Mount the PCB with M3 nylon screws or insulated spacers. Ensure that any metal parts outside the box are not connected to any metal parts inside the box.

When fitting the lid onto the box, ensure the wires do not lay underneath the PCB. A suitable front panel overlay is shown in Figure 3. This may be photocopied and fixed to the case with clear self adhesive vinyl.

Testing

NEVER OPERATE THIS UNIT UNLESS IT IS FULLY ASSEMBLED. MAINS VOLTAGE CAN KILL - PLEASE BE VERY CAREFUL!

If the unit is correctly assembled there is no reason why it should not work first time. If a residual current (earth leakage) circuit breaker is available, it would be

sensible to plug the testplug into this for initial testing. Assuming your socket is wired correctly, the outer two neons should light and the centre one should remain off.

If you wish to try the various fault conditions, this can be achieved by altering the wiring in one end of an extension lead. Switch the mains off and unplug before touching any connections, and replace all covers before switching back on. Be sure to rewire the extension lead correctly when finished.


In Use

Using the testplug is extremely straightforward. Simply plug it into the socket, if the outer neons light the socket is wired correctly. If any other combination of neons illuminate, there is a fault with the socket which must be investigated. A faulty socket must not be used under any circumstances.

When testing extension leads and multiway adaptors, wiggle the test plug around and check that the neons do not flicker. Many multiway adaptors have poor earth contacts which can give intermittent operation.

Never take any chances with mains electricity. If you are in any doubt, please seek expert advice.

Fig.3 Front panel design

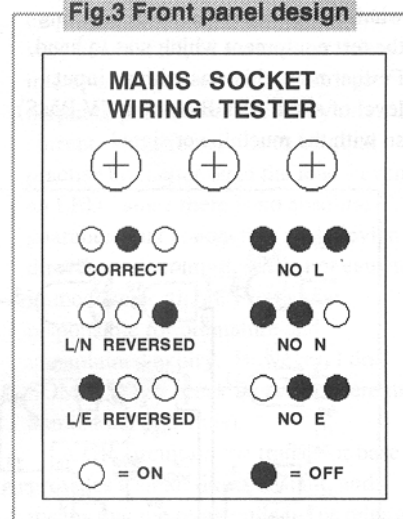

Resistors

R1,3,5 100K 0.25W

R2,4,6 220K 0.25W

Additional Components

N1,2,3 Wire Ended Neon Lamp PCB

13A Plug (see text)

3A Fuse

Box Type T3

3A Three Core Mains Flex

M3 Screws Nuts and Spacers

Cable Tie

Parts